

Charles Tung Fang

EE 271

Professor Rania Hussein

## Lab 4 Report

### Procedure

In order to understand the whole project and know where to start, I began with drawing the top-level block diagram for my entire design (Figure 1). The whole diagram is my DE1\_SoC module and in that I called userInput and playField.

First, I dealt with the metastability in the metastability function. With the output from metastability, I then used it to count the key press. The key press is counted as one when it is pressed then released (Figure 2).

Second, I passed in the L and R output from the previous action into the playField module. In the playField function I called eight normalLight modules representing LEDR1~LEDR4 and LEDR6~LEDR9. I also called centerLight module representing LEDR5. After calling the lights, I have the victory module to determine the winner and show the winner on the HEX0.

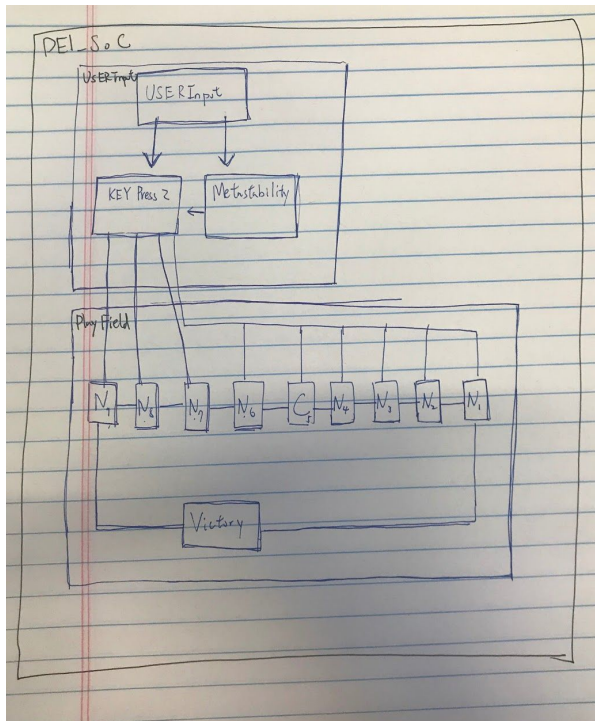


Figure 1. Block Diagram



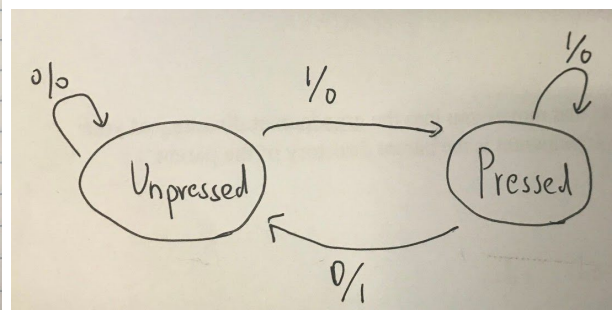



Figure 2. Key Pressed FSM

After implementing each module, I tested every single one of them on the modelSim before I combined them all together. I made sure every module behaved the way they're expected through the modelSim. I tested larger modules, userInput and playField (Figure 3, Figure 4), to make sure inputs got modified and pass on. In the end, I tested the DE1\_SoC (Figure 5) and wrote a testbench for player 1 & 2 to win each time in order to confirm if different LEDR values changed, and if ultimately the HEX0 showed the winner.

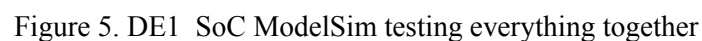


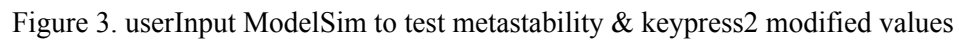


## Appendix

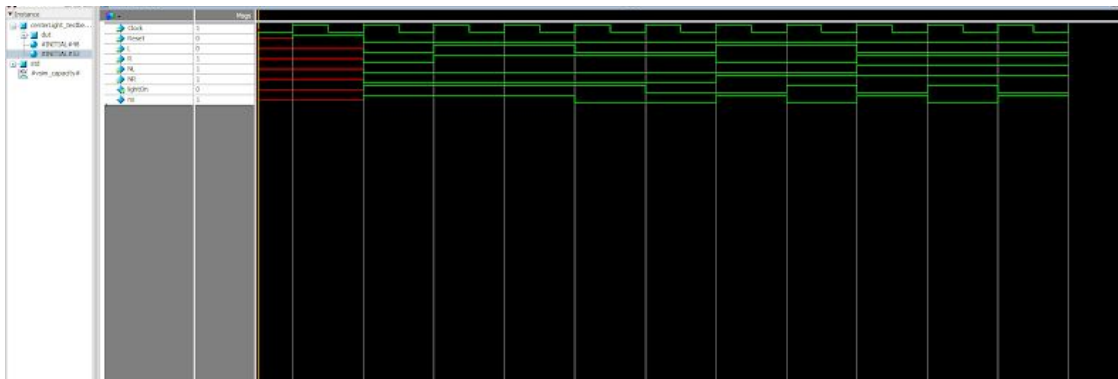


ModelSim for CenterLight

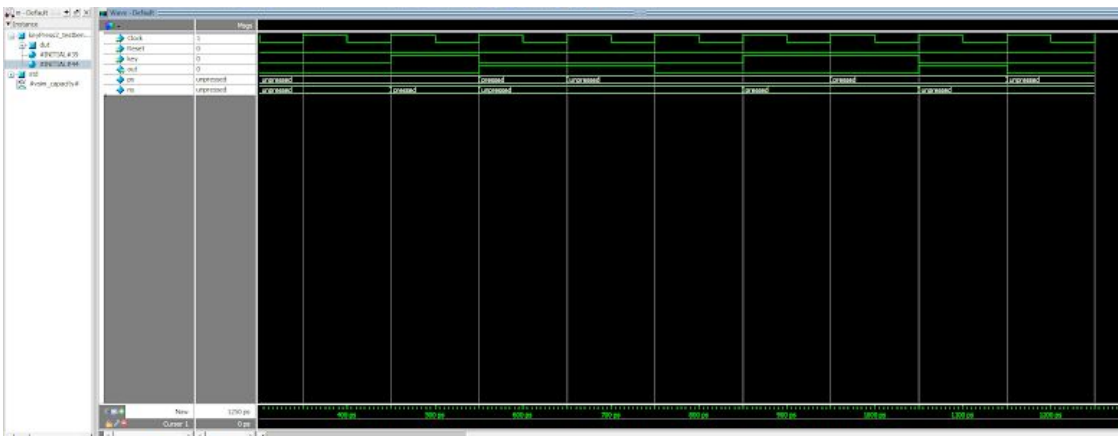


ModelSim for KeyPress2

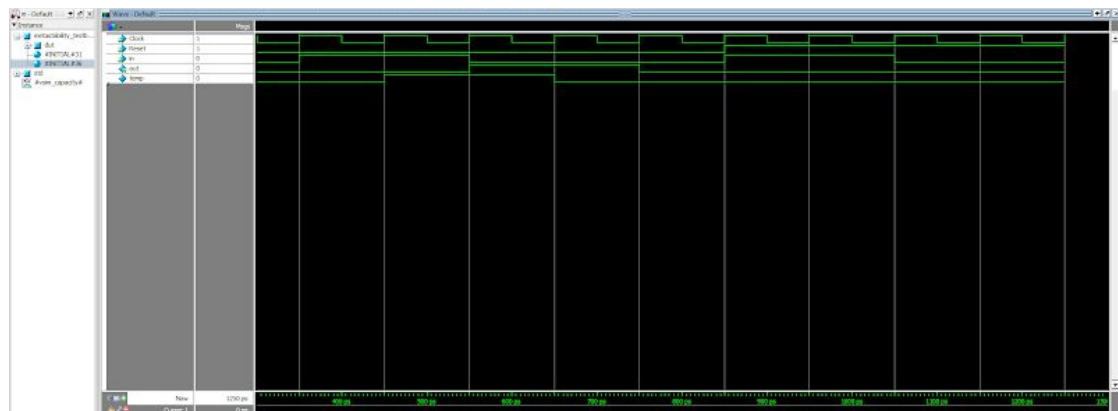

ModelSim for Metastability

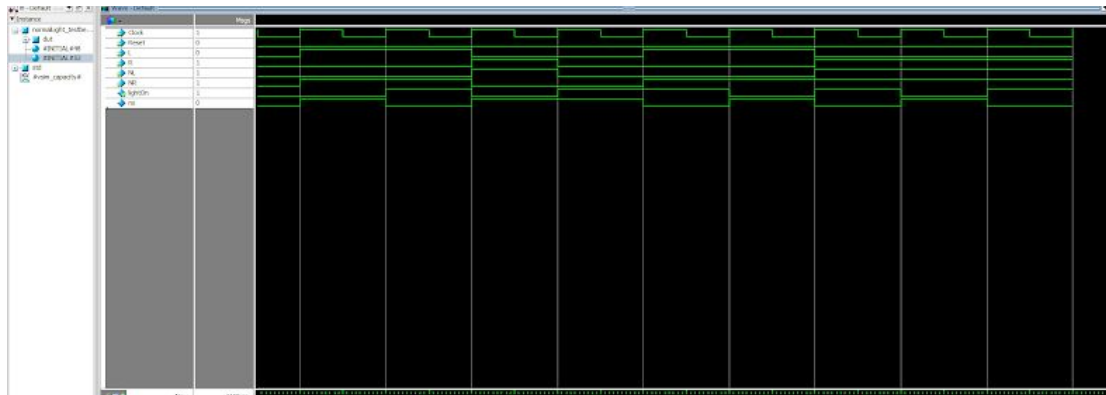

## ModelSim for normalLight

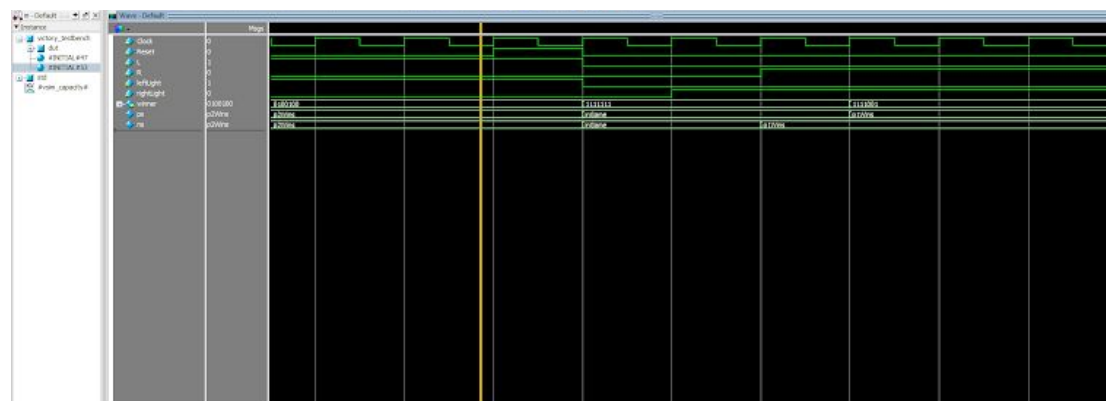

ModelSim for Victory